

## EXPERIMENT 4:

### Thévenin Equivalent Circuit and Maximum Power Transfer

#### Objective:

Verify Thévenin's theorem by obtaining the Thévenin equivalent voltage ( $V_{TH}$ ) and Thévenin equivalent resistance ( $R_{TH}$ ) for the given circuit. Verify the Maximum Power Transfer Theorem.

#### Equipment:

- Circuit Board
- Assorted Resistors(300  $\Omega$  (2), 560  $\Omega$  (2), 820  $\Omega$  and 1.2 K $\Omega$ )
- Decade Resistance Box.

#### Theory:

**Thévenin's Theorem:** It is a process by which a complex circuit is reduced to an equivalent series circuit consisting of a single voltage source ( $V_{TH}$ ), a series resistance ( $R_{TH}$ ) and a load resistance ( $R_L$ ). After creating the Thévenin Equivalent Circuit, the load voltage  $V_L$  or the load current  $I_L$  may be easily determined.

One of the main uses of Thévenin's theorem is the replacement of a large part of a circuit, often a complicated and uninteresting part, by a very simple equivalent. The new simpler circuit enables us to make rapid calculations of the voltage, current, and power which the original circuit is able to deliver to a load. It also helps us to choose the best value of this load resistance for *maximum* power transfer.

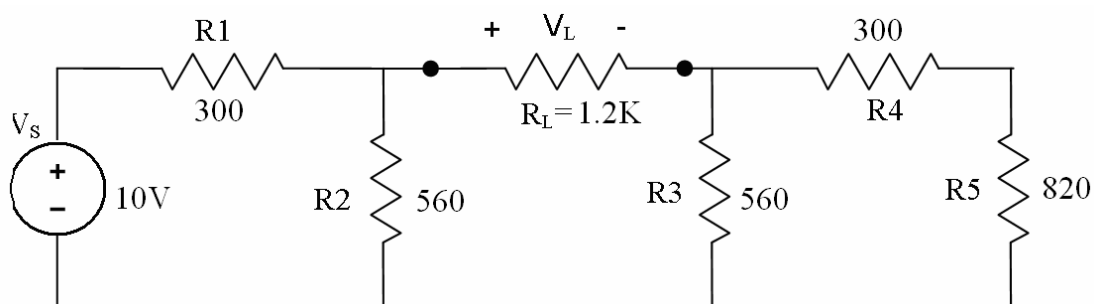


Figure 1.

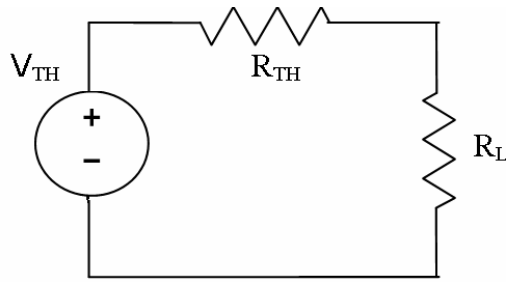


Figure 2: Thévenin Equivalent Circuit of Figure 1

2. **Maximum Power Transfer Theorem** states that an independent voltage source in series with a resistance  $R_S$  or an independent current source in parallel with a resistance  $R_S$ , delivers a maximum power to that load resistance  $R_L$  for which  $R_L = R_S$ .

In terms of a Thévenin Equivalent Circuit, maximum power is delivered to the load resistance  $R_L$  when  $R_L$  is equal to the Thévenin equivalent resistance  $R_{TH}$  of the circuit.


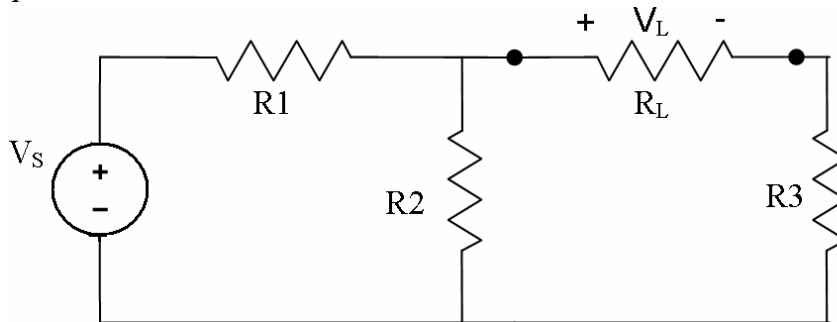


Figure 3: Maximum Power Transfer

**Procedure:**


1. Verifying the Thévenin's theorem:
  - a) Construct the circuit of Figure 1 using the following component values:
    - $R_1 = 300 \Omega$
    - $R_2 = 560 \Omega$
    - $R_3 = 560 \Omega$
    - $R_4 = 300 \Omega$
    - $R_5 = 820 \Omega$
    - $R_L = 1.2 \text{ K}\Omega$
    - $V_S = 10 \text{ V}$
  - b) Accurately measure the voltage  $V_L$  across the load resistance using NI Elvis voltmeter or an external DMM. This value will later be compared to the one you will find using Thevenin Equivalent.

- c) Find  $V_{TH}$ : Remove the load resistance  $R_L$  and measure the open circuit voltage  $V_{OC}$  across the terminals. This is equal to  $V_{TH}$ . See Figure 4. below

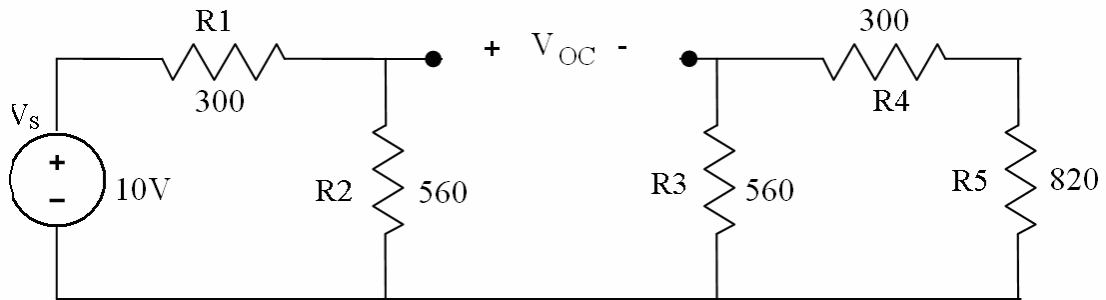


**Figure 4: Measuring the Thevenin Voltage**

- d) Find  $R_{TH}$ : Remove the source voltage  $V_S$  and construct the circuit as in Fig.5.. below. Measure the resistance looking into the opening where  $R_L$  was with an ohmmeter (DMM). This gives  $R_{TH}$ . Make sure there is no power in the circuit before measuring with an Ohm-meter.

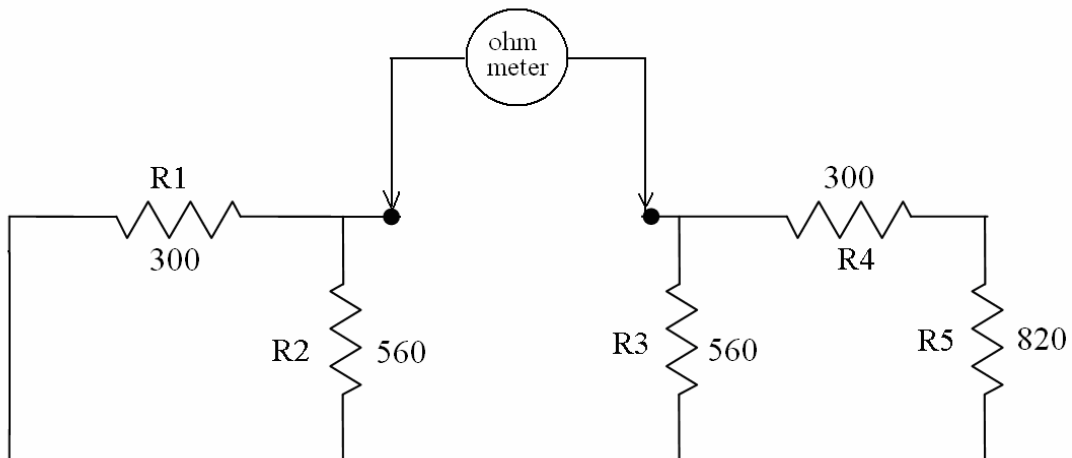

**Figure 5: Measuring the Thevenin Resistance  $R_{TH}$ .**

- e) Obtaining  $V_{TH}$  and  $R_{TH}$ , construct the circuit of figure 2. Set the value of  $R_{TH}$  using a Decade Resistance Box, and set  $V_{TH}$  using variable power supply.

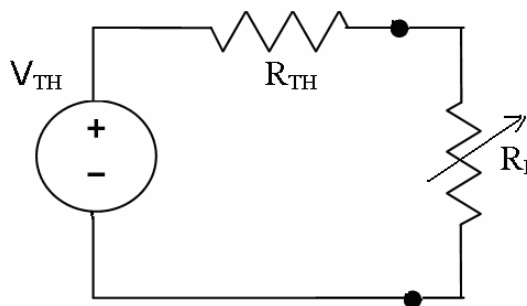


**Figure 6: Thevenin Equivalent Construction**

- f) Measure the  $V_L$  for this circuit and compare it to the  $V_L$  obtained in Procedure 1-b. This verifies the Thévenin theorem.
- g) Optional: Repeat steps 1(b) to 1(f) for  $R_L = 3.3 \text{ K}\Omega$

2. Verifying the Maximum Power Transfer theorem:

- a) Construct the circuit as in Figure 7 using the following values:  
 $V_S = 10 \text{ V}$   
 $R_1 = R_2 = 560 \Omega$   
 $R_3 = 820 \Omega$   
 $R_L = \text{Decade Resistance Box (DRB)}$

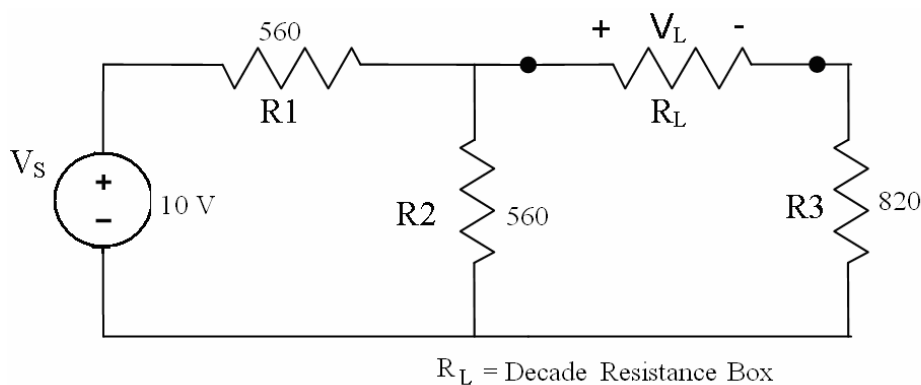

**Figure 7: Circuit for Max. Pow. Theorem**

- b) Connect the DMM across  $R_L$  for measuring the load voltage.
- c) To find the value of  $R_L$  for which maximum power is transferred, vary the resistances on the DRB between  $800 \Omega$  to  $1400 \Omega$  in  $100 \Omega$  steps and note down  $V_L$  for each case.
- d) Calculate the power for each load resistor value (DRB) using  $P_L = V_L^2 / R_L$ . Then, find the resistor value corresponding to the maximum power ( $P_{L-\max}$ ). This value should be equal to  $R_{TH}$  of circuit in fig.7 with respect to load terminals.

**Questions for Lab Report:**

1. Calculate the percentage error difference between the load voltages obtained for circuits of figure 1 and figure 2.
2. Using Voltage Division for circuit of figure 2, calculate  $V_L$ . Compare it to the measured values. Explain any differences.
3. Calculate the maximum power transmitted to the load  $R_L$  obtained for the circuit of figure 3.